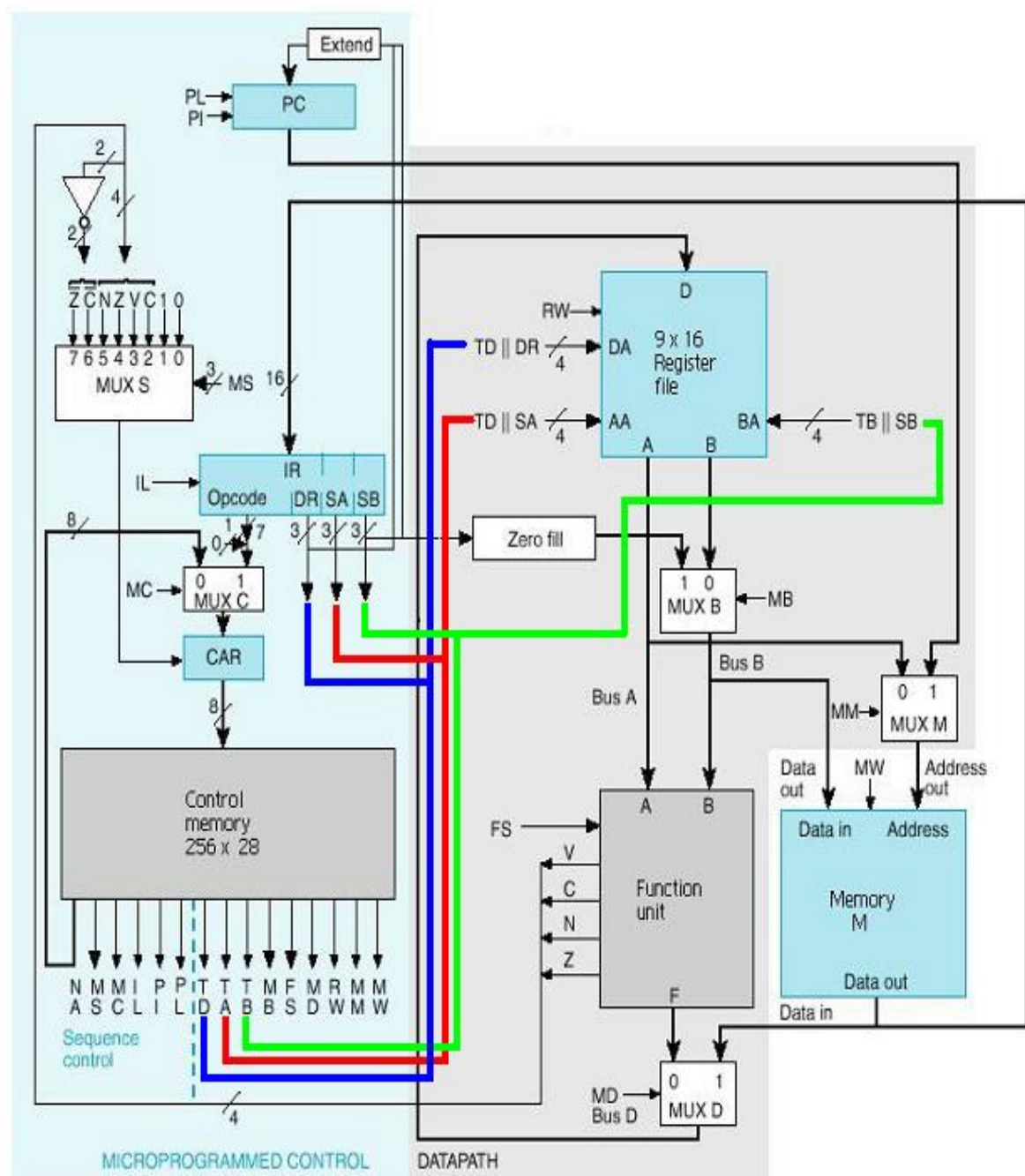


TADHG RIORDAN  
12309240  
ASSIGNMENT 3: COMPUTER ARCHITECHTURE  
MICROCODED INSTRUCTION SET PROCESSOR

I will show the components for the microcoded instruction set processor component by component, along with a testbench for each and a short comment on how it works. While each component individually works as specified and I have a ,processor' file which connects them together, I could not in the end get the microcoded instructions work. I believe that I would eventually work this out if I had more time, but underestimated the degree of work in debugging the connected components. The overall Datapath (assignment 2) and register file(assignment 1) work perfectly however and I will specify these also.



### PROGRAM COUNTER:

The program counter works by the control of the PI and PL signals. PI will increment it and PL will add it to the enable output and load it.

#### CODE:

```
entity Program_counter is
  Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
         reset : IN std_logic;
         PI : in  STD_LOGIC;
         PL : in  STD_LOGIC;
         Clk : in  STD_LOGIC;
         out0 : inout STD_LOGIC_VECTOR(15 DOWNTO 0)
        );
end Program_counter;

architecture Behavioral of Program_counter is

  component Arith_fullAdder
  Port (
    X : in  STD_LOGIC;
    Y : in  STD_LOGIC;
    Cin : in  STD_LOGIC;
    Cout : out STD_LOGIC;
    Gout : out STD_LOGIC);
  end component;

  signal p, PICout_sig, PIGout_sig, PLCout_sig, PLGout_sig
  :std_logic_vector(15 downto 0);
  signal temp : std_logic_vector(1 downto 0);
begin
  --PI PORT MAPS
  PI00:Arith_fullAdder PORT MAP (
    X => out0(0),
    Y => '1',
    Cin => '0',
    Cout => PICout_sig(0),
    Gout => PIGout_sig(0)
  );

  PI01:Arith_fullAdder PORT MAP(
    X => out0(1),
    Y => '0',
    Cin => PICout_sig(0),
    Cout => PICout_sig(1),
    Gout => PIGout_sig(1)
  );

  PI02:Arith_fullAdder PORT MAP(
    X => out0(2),
    Y => '0',
    Cin => PICout_sig(1),
    Cout => PICout_sig(2),
    Gout => PIGout_sig(2)
  );

  PI03:Arith_fullAdder PORT MAP(
    X => out0(3),
    Y => '0',
    Cin => PICout_sig(2),
    Cout => PICout_sig(3),
    Gout => PIGout_sig(3)
  );
```

```

    PI04:Arith_fullAdder PORT MAP(
X => out0(4),
Y => '0',
Cin => PICout_sig(3),
Cout => PICout_sig(4),
Gout => PIGout_sig(4)
);

    PI05:Arith_fullAdder PORT MAP(
X => out0(5),
Y => '0',
Cin => PICout_sig(4),
Cout => PICout_sig(5),
Gout => PIGout_sig(5)
);

    PI06:Arith_fullAdder PORT MAP(
X => out0(6),
Y => '0',
Cin => PICout_sig(5),
Cout => PICout_sig(6),
Gout => PIGout_sig(6)
);

    PI07:Arith_fullAdder PORT MAP(
X => out0(7),
Y => '0',
Cin => PICout_sig(6),
Cout => PICout_sig(7),
Gout => PIGout_sig(7)
);

    PI08:Arith_fullAdder PORT MAP(
X => out0(8),
Y => '0',
Cin => PICout_sig(7),
Cout => PICout_sig(8),
Gout => PIGout_sig(8)
);

    PI09:Arith_fullAdder PORT MAP(
X => out0(9),
Y => '0',
Cin => PICout_sig(8),
Cout => PICout_sig(9),
Gout => PIGout_sig(9)
);

    PI10:Arith_fullAdder PORT MAP(
X => out0(10),
Y => '0',
Cin => PICout_sig(9),
Cout => PICout_sig(10),
Gout => PIGout_sig(10)
);

    PI11:Arith_fullAdder PORT MAP(
X => out0(11),
Y => '0',
Cin => PICout_sig(10),
Cout => PICout_sig(11),
Gout => PIGout_sig(11)
);

```

```

);

    PI12:Arith_fullAdder PORT MAP(
X => out0(12),
Y => '0',
Cin => PICout_sig(11),
Cout => PICout_sig(12),
Gout => PIGout_sig(12)
);

    PI13:Arith_fullAdder PORT MAP(
X => out0(13),
Y => '0',
Cin => PICout_sig(12),
Cout => PICout_sig(13),
Gout => PIGout_sig(13)
);

    PI14:Arith_fullAdder PORT MAP(
X => out0(14),
Y => '0',
Cin => PICout_sig(13),
Cout => PICout_sig(14),
Gout => PIGout_sig(14)
);

    PI15:Arith_fullAdder PORT MAP(
X => out0(15),
Y => '0',
Cin => PICout_sig(14),
Cout => PICout_sig(15),
Gout => PIGout_sig(15)
);

    --PL port maps
    PL00:Arith_fullAdder PORT MAP (
X => out0(0),
Y => in0(0),
Cin => '0',
Cout => PLCout_sig(0),
Gout => PLGout_sig(0)
);

    PL01:Arith_fullAdder PORT MAP(
X => out0(1),
Y => in0(1),
Cin => PLCout_sig(0),
Cout => PLCout_sig(1),
Gout => PLGout_sig(1)
);

    PL02:Arith_fullAdder PORT MAP(
X => out0(2),
Y => in0(2),
Cin => PLCout_sig(1),
Cout => PLCout_sig(2),
Gout => PLGout_sig(2)
);

    PL03:Arith_fullAdder PORT MAP(
X => out0(3),
Y => in0(3),
Cin => PLCout_sig(2),

```

```

Cout => PLCout_sig(3),
Gout => PLGout_sig(3)
);

    PL04:Arith_fullAdder PORT MAP(
X => out0(4),
Y => in0(4),
Cin => PLCout_sig(3),
Cout => PLCout_sig(4),
Gout => PLGout_sig(4)
);

    PL05:Arith_fullAdder PORT MAP(
X => out0(5),
Y => in0(5),
Cin => PLCout_sig(4),
Cout => PLCout_sig(5),
Gout => PLGout_sig(5)
);

    PL06:Arith_fullAdder PORT MAP(
X => out0(6),
Y => in0(6),
Cin => PLCout_sig(5),
Cout => PLCout_sig(6),
Gout => PLGout_sig(6)
);

    PL07:Arith_fullAdder PORT MAP(
X => out0(7),
Y => in0(7),
Cin => PLCout_sig(6),
Cout => PLCout_sig(7),
Gout => PLGout_sig(7)
);

    PL08:Arith_fullAdder PORT MAP(
X => out0(8),
Y => in0(8),
Cin => PLCout_sig(7),
Cout => PLCout_sig(8),
Gout => PLGout_sig(8)
);

    PL09:Arith_fullAdder PORT MAP(
X => out0(9),
Y => in0(9),
Cin => PLCout_sig(8),
Cout => PLCout_sig(9),
Gout => PLGout_sig(9)
);

    PL10:Arith_fullAdder PORT MAP(
X => out0(10),
Y => in0(10),
Cin => PLCout_sig(9),
Cout => PLCout_sig(10),
Gout => PLGout_sig(10)
);

    PL11:Arith_fullAdder PORT MAP(
X => out0(11),
Y => in0(11),

```

```

    Cin => PLCout_sig(10),
    Cout => PLCout_sig(11),
    Gout => PLGout_sig(11)
);

    PL12:Arith_fullAdder PORT MAP(
X => out0(12),
Y => in0(12),
Cin => PLCout_sig(11),
Cout => PLCout_sig(12),
Gout => PLGout_sig(12)
);

    PL13:Arith_fullAdder PORT MAP(
X => out0(13),
Y => in0(13),
Cin => PLCout_sig(12),
Cout => PLCout_sig(13),
Gout => PLGout_sig(13)
);

    PL14:Arith_fullAdder PORT MAP(
X => out0(14),
Y => in0(14),
Cin => PLCout_sig(13),
Cout => PLCout_sig(14),
Gout => PLGout_sig(14)
);

    PL15:Arith_fullAdder PORT MAP(
X => out0(15),
Y => in0(15),
Cin => PLCout_sig(14),
Cout => PLCout_sig(15),
Gout => PLGout_sig(15)
);
process(Clk)
begin

if(rising_edge(Clk)) then
    if reset = '1' then out0 <= "0000000000000000";
    elsif PI = '1' then out0 <= PIGout_sig;
    elsif PL = '1' then out0 <= PLGout_sig;
    end if;
end if;
end process;
end Behavioral;

```

## TESTBENCH:

```

ENTITY program_counterTest IS
END program_counterTest;

```

```

ARCHITECTURE behavior OF program_counterTest IS

```

```

    -- Component Declaration for the Unit Under Test
    (UUT)

```

```

COMPONENT Program_counter
PORT(
    in0 : IN    std_logic_vector(15 downto 0);
        reset : IN std_logic;
    PI : IN    std_logic;
    PL : IN    std_logic;
    Clk : IN    std_logic;
    out0 : inout std_logic_vector(15 downto 0)
);
END COMPONENT;

--Inputs
signal in0 : std_logic_vector(15 downto 0) :=
(others => '0');
    signal reset : std_logic := '0';
signal PI : std_logic := '0';
signal PL : std_logic := '0';
signal Clk : std_logic := '0';

--Outputs
signal out0 : std_logic_vector(15 downto 0);

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Program_counter PORT MAP (
        in0 => in0,
        reset => reset,
        PI => PI,
        PL => PL,
        Clk => Clk,
        out0 => out0
    );

    -- Clock process definitions
    Clk_process :process
begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
end process;

```



```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    --wait for Clk_period*10;
    reset <= '1';
    wait for 5ns;
    reset <= '0';
    --out0 <= "000000000000000000";
    --in0 <= "000000000000000010";

    --PI <= '1';
    --wait for 10ns;
    --assert out0 = "000000000000000001";
    --PI <= '0';
    --wait for 10ns;

    reset <= '1';
    wait for 10ns;
    reset <= '0';

    --PI <= '0';
    --wait for 10ns;

    --PL <= '1';
    --wait for 10ns;
    --assert out0 = "000000000000000010";

    wait;
end process;

END;

```

## ENTITY

## CODE

```

entity extend is
    Port ( in0 : in  STD_LOGIC_VECTOR(5 DOWNTO 0);
          out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
          );
end extend;

architecture Behavioral of extend is

begin
process(in0(5))

```

```

begin
  if in0(5) = '1' then
    out0(15 downto 6) <= "1111111111";
    out0(5 downto 0) <= in0;
  elsif in0(5) = '0' then
    out0(15 downto 6) <= "0000000000";
    out0(5 downto 0) <= in0;
  end if;
end process;
end Behavioral;

```

## TESTBENCH

```

ENTITY extendTest IS
END extendTest;

```

```

ARCHITECTURE behavior OF extendTest IS

```

```

    -- Component Declaration for the Unit Under Test
    (UUT)

```

```

    COMPONENT extend
    PORT(
        in0 : IN  std_logic_vector(5 downto 0);
        out0 : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

```

```

    --Inputs
    signal in0 : std_logic_vector(5 downto 0) :=
    (others => '0');

```

```

    --Outputs
    signal out0 : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

```

```

    --constant <clock>_period : time := 10 ns;

```

```

BEGIN

```

```

    -- Instantiate the Unit Under Test (UUT)
    uut: extend PORT MAP (
        in0 => in0,
        out0 => out0
    );

```

```

    );

-- Clock process definitions
--<clock>_process :process
--begin
    --<clock> <= '0';
    --wait for <clock>_period/2;
    --<clock> <= '1';
    --wait for <clock>_period/2;
--end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    in0 <= "101010";
    wait for 10ns;
    assert out0 = "1111111111101010";

    in0 <= "001010";
    wait for 10ns;
    assert out0 = "0000000000001010";

    --wait for <clock>_period*10;
    -- insert stimulus here

    wait;
end process;

END;

```

## MEMORY

## CODE

```

entity Memory is -- use unsigned for memory address
Port ( address : in unsigned(15 downto 0);
       write_data : in std_logic_vector(15 downto
0);
       MW : in std_logic;
       read_data : out std_logic_vector(15 downto
0));
end Memory;

```

**architecture** Behavioral **of** Memory **is**

```
type mem_array is array(0 to 511) of  
std_logic_vector(15 downto 0); -- define type, for  
memory arrays
```

**begin**

```
mem_process: process (address, write_data, MW)
-- initialize data memory, X denotes hexadecimal
number
```

[illegible]

[illegible]



```

if MW = '1' then
data_mem(addr) := write_data;
elsif MW = '0' then
read_data <= data_mem(addr) after 10 ns;
end if;
end process;
end Behavioral;

```

## **TESTBENCH**

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;

```

```

-- Uncomment the following library declaration if
using
-- arithmetic functions with Signed or Unsigned
values
--USE ieee.numeric_std.ALL;

```

```

ENTITY MemoryTest IS
END MemoryTest;

```

```

ARCHITECTURE behavior OF MemoryTest IS

```

```

    -- Component Declaration for the Unit Under Test
    (UUT)

```

```

    COMPONENT Memory
    PORT(
        address : IN   unsigned(15 downto 0);
        write_data : IN   std_logic_vector(15 downto
0);
        MW : IN   std_logic;
        read_data : OUT   std_logic_vector(15 downto
0)
    );
    END COMPONENT;

```

```

    --Inputs
    signal address : unsigned(15 downto 0) := (others
=> '0');
    signal write_data : std_logic_vector(15 downto 0)
:= (others => '0');
    signal MW : std_logic := '0';

```

```

    --Outputs
    signal read_data : std_logic_vector(15 downto 0)
:= (others => '0');
    -- No clocks detected in port list. Replace
<clock> below with
    -- appropriate port name

    --constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Memory PORT MAP (
        address => address,
        write_data => write_data,
        MW => MW,
        read_data => read_data
    );

    -- Clock process definitions
    --<clock>_process :process
    --begin
        --<clock> <= '0';
        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

    -- Stimulus process
    stim_proc: process
begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        address <= "0000000000000000";
        MW <= '0';
        wait for 100ns;

        write_data <= "0000000000001111";
        MW <= '1';
        wait for 100ns;

        MW <= '0';
        wait for 10ns;
        assert read_data = "0000000000001111";

        --wait for <clock>_period*10;

```



```

        -- insert stimulus here

        wait;
    end process;

END;

```

## INVERTER

### CODE

```

entity NOT_cond is
    Port ( in0 : in  STD_LOGIC;
           in1 : in  STD_LOGIC;
           out0 : out STD_LOGIC;
           out1 : out STD_LOGIC);
end NOT_cond;

architecture Behavioral of NOT_cond is

begin
    out0 <= not(in0);
    out1 <= not(in1);

end Behavioral;

TESTBENCH

ENTITY not_condTest IS
END not_condTest;

ARCHITECTURE behavior OF not_condTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT NOT_cond
    PORT(
        in0 : IN  std_logic;
        in1 : IN  std_logic;
        out0 : OUT std_logic;
        out1 : OUT std_logic
    );

```

```

END COMPONENT;

--Inputs
signal in0 : std_logic := '0';
signal in1 : std_logic := '0';

--Outputs
signal out0 : std_logic;
signal out1 : std_logic;
-- No clocks detected in port list. Replace
<clock> below with
-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)
uut: NOT_cond PORT MAP (
    in0 => in0,
    in1 => in1,
    out0 => out0,
    out1 => out1
);

-- Clock process definitions
--<clock>_process :process
--begin
--<clock> <= '0';
--wait for <clock>_period/2;
--<clock> <= '1';
--wait for <clock>_period/2;
--end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    in0 <= '0';
    in1 <= '1';
    wait for 5ns;
    assert out0 <= '1';
    assert out1 <= '0';

```

```

        wait;
    end process;

END;

MUX_S

CODE
entity MUX_S is
    Port ( in0 : in  STD_LOGIC;
           in1 : in  STD_LOGIC;
           in2 : in  STD_LOGIC;
           in3 : in  STD_LOGIC;
           in4 : in  STD_LOGIC;
           in5 : in  STD_LOGIC;
           in6 : in  STD_LOGIC;
           in7 : in  STD_LOGIC;
           sel : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
           out0 : out STD_LOGIC
        );
end MUX_S;

architecture Behavioral of MUX_S is

begin
    out0 <= in0 when sel = "000" else
            in1 when sel = "001" else
            in2 when sel = "010" else
            in3 when sel = "011" else
            in4 when sel = "100" else
            in5 when sel = "101" else
            in6 when sel = "110" else
            in7 when sel = "111" else
            'U' after 5ns;

end Behavioral;

TESTBENCH
ENTITY MUX_STest IS
END MUX_STest;

ARCHITECTURE behavior OF MUX_STest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT MUX_S
    PORT(

```

```

        in0 : IN    std_logic;
        in1 : IN    std_logic;
        in2 : IN    std_logic;
        in3 : IN    std_logic;
        in4 : IN    std_logic;
        in5 : IN    std_logic;
        in6 : IN    std_logic;
        in7 : IN    std_logic;
        sel : IN    std_logic_vector(2 downto 0);
        out0 : OUT   std_logic
    );
END COMPONENT;

--Inputs
signal in0 : std_logic := '0';
signal in1 : std_logic := '0';
signal in2 : std_logic := '0';
signal in3 : std_logic := '0';
signal in4 : std_logic := '0';
signal in5 : std_logic := '0';
signal in6 : std_logic := '0';
signal in7 : std_logic := '0';
signal sel : std_logic_vector(2 downto 0) :=
(others => '0');

--Outputs
signal out0 : std_logic;
-- No clocks detected in port list. Replace
<clock> below with
-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: MUX_S PORT MAP (
        in0 => in0,
        in1 => in1,
        in2 => in2,
        in3 => in3,
        in4 => in4,
        in5 => in5,
        in6 => in6,
        in7 => in7,
        sel => sel,
        out0 => out0

```

```

    );

-- Clock process definitions
--<clock>_process :process
--begin
    --<clock> <= '0';
    --wait for <clock>_period/2;
    --<clock> <= '1';
    --wait for <clock>_period/2;
--end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    in0 <= '0';
    in1 <= '1';
    in2 <= '0';
    in3 <= '1';
    in4 <= '0';
    in5 <= '1';
    in6 <= '0';
    in7 <= '1';

    sel <= "000";
    wait for 10ns;
    assert out0 = '0';

    sel <= "001";
    wait for 10ns;
    assert out0 = '1';

    sel <= "010";
    wait for 10ns;
    assert out0 = '0';

    sel <= "011";
    wait for 10ns;
    assert out0 = '1';

    sel <= "100";
    wait for 10ns;
    assert out0 = '0';

    sel <= "101";
    wait for 10ns;

```

```

        assert out0 = '1';

        sel <= "110";
        wait for 10ns;
        assert out0 = '0';

        sel <= "111";
        wait for 10ns;
        assert out0 = '1';

        --wait for <clock>_period*10;

        -- insert stimulus here

        wait;
    end process;

END;

INSTRUCTION REGISTER

CODE
entity Instruction_reg is
    Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
          sel : in  STD_LOGIC;
          opcode : out  STD_LOGIC_VECTOR(6 DOWNTO
0);
          DR : out  STD_LOGIC_VECTOR(2 DOWNTO 0);
          SA : out  STD_LOGIC_VECTOR(2 DOWNTO 0);
          Clk : in  STD_LOGIC;
          SB : out  STD_LOGIC_VECTOR(2 DOWNTO 0)
          );
end Instruction_reg;

architecture Behavioral of Instruction_reg is
begin
    process(Clk)
    begin
        if(rising_edge(Clk)) then
            if sel = '1' then
                opcode <= in0(15 downto 9);
                DR <= in0(8 downto 6);
                SA <= in0(5 downto 3);
                SB <= in0(2 downto 0);
            end if;
        end if;
    end process;
end Behavioral;

```

```

TESTBENCH
ENTITY InstructionRegTest IS
END InstructionRegTest;

ARCHITECTURE behavior OF InstructionRegTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT Instruction_reg
    PORT(
        in0 : IN  std_logic_vector(15 downto 0);
        sel : IN  std_logic;
        opcode : OUT std_logic_vector(6 downto 0);
        DR : OUT  std_logic_vector(2 downto 0);
        SA : OUT  std_logic_vector(2 downto 0);
        Clk : IN  std_logic;
        SB : OUT  std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal in0 : std_logic_vector(15 downto 0) :=
    (others => '0');
    signal Clk : std_logic := '0';
    signal sel : std_logic := '0';

    --Outputs
    signal opcode : std_logic_vector(6 downto 0);
    signal DR : std_logic_vector(2 downto 0);
    signal SA : std_logic_vector(2 downto 0);
    signal SB : std_logic_vector(2 downto 0);

    -- Clock period definitions
    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Instruction_reg PORT MAP (
        in0 => in0,
        Clk => Clk,
        sel => sel,
        opcode => opcode,
        DR => DR,
        SA => SA,

```

```

        SB => SB
    );

-- Clock process definitions
Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    in0 <= "0101010101010101";
    sel <= '0';
    wait for 10ns;
    assert opcode = "UUUUUUUU";
    assert DR = "UUU";
    assert SA = "UUU";
    assert SB = "UUU";

    sel <= '1';
    wait for 10ns;
    assert opcode = "0101010";
    assert DR = "101";
    assert SA = "010";
    assert SB = "101";

    sel <= '0';
    wait for 10ns;
    assert opcode = "0101010";
    assert DR = "101";
    assert SA = "010";
    assert SB = "101";

    in0 <= "1111111111111111";
    wait for 10ns;
    assert opcode = "0101010";
    assert DR = "101";
    assert SA = "010";
    assert SB = "101";

```



```

        sel <= '1';
        wait for 10ns;
        assert opcode = "1111111";
        assert DR = "111";
        assert SA = "111";
        assert SB = "111";

        wait for Clk_period*10;
        -- insert stimulus here

        wait;
    end process;

END;

MUX_C

CODE
entity MUX_C is
    Port ( in0 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
          in1 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
          sel : in  STD_LOGIC;
          out0 : out STD_LOGIC_VECTOR(7 DOWNTO 0)
        );
end MUX_C;

architecture Behavioral of MUX_C is

begin
    out0 <= in0 when sel = '0' else
            in1 when sel = '1' else
            "UUUUUUUU" after 5ns;

end Behavioral;

TESTBENCH

ENTITY MUXCTest IS
END MUXCTest;

ARCHITECTURE behavior OF MUXCTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT MUX_C
    PORT(
        in0 : IN  std_logic_vector(7 downto 0);

```

```

        in1 : IN  std_logic_vector(7 downto 0);
        sel : IN  std_logic;
        out0 : OUT std_logic_vector(7 downto 0)
    );
END COMPONENT;

--Inputs
    signal in0 : std_logic_vector(7 downto 0) :=
( others => '0' );
    signal in1 : std_logic_vector(7 downto 0) :=
( others => '0' );
    signal sel : std_logic := '0';

--Outputs
    signal out0 : std_logic_vector(7 downto 0);
    -- No clocks detected in port list. Replace
<clock> below with
    -- appropriate port name

    --constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: MUX_C PORT MAP (
        in0 => in0,
        in1 => in1,
        sel => sel,
        out0 => out0
    );

    -- Clock process definitions
    --<clock>_process :process
    --begin
        --<clock> <= '0';
        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        in0 <= "00000000";

```

```

        in1 <= "11111111";

        sel <= '0';
        wait for 10ns;
        assert out0 <= "00000000";

        sel <= '1';
        wait for 10ns;
        assert out0 <= "11111111";

        --wait for <clock>_period*10;
        -- insert stimulus here

        wait;
    end process;

END;

CONTROL ACCESS REGISTER (CAR)

CODE
entity control_access_reg is
    Port ( in0 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
          Clk : in  STD_LOGIC;
          reset : in STD_LOGIC;
          sel : in  STD_LOGIC;
          out0 : inout STD_LOGIC_VECTOR(7 DOWNTO 0)
          );
end control_access_reg;

architecture Behavioral of control_access_reg is

    component Arith_fullAdder
    Port (
        X : in  STD_LOGIC;
        Y : in  STD_LOGIC;
        Cin : in  STD_LOGIC;
        Cout : out STD_LOGIC;
        Gout : out STD_LOGIC);
    end component;

    --signals
    signal Cout_sig, Gout_sig : STD_LOGIC_VECTOR(7 DOWNTO 0);

    begin
        CAR00:Arith_fullAdder PORT MAP(
            X => out0(0),
            Y => '1',

```

```

Cin => '0',
Cout => Cout_sig(0),
Gout => Gout_sig(0)
);

CAR01:Arith_fullAdder PORT MAP(
X => out0(1),
Y => '0',
Cin => Cout_sig(0),
Cout => Cout_sig(1),
Gout => Gout_sig(1)
);

CAR02:Arith_fullAdder PORT MAP(
X => out0(2),
Y => '0',
Cin => Cout_sig(1),
Cout => Cout_sig(2),
Gout => Gout_sig(2)
);

CAR03:Arith_fullAdder PORT MAP(
X => out0(3),
Y => '0',
Cin => Cout_sig(2),
Cout => Cout_sig(3),
Gout => Gout_sig(3)
);

CAR04:Arith_fullAdder PORT MAP(
X => out0(4),
Y => '0',
Cin => Cout_sig(3),
Cout => Cout_sig(4),
Gout => Gout_sig(4)
);

CAR05:Arith_fullAdder PORT MAP(
X => out0(5),
Y => '0',
Cin => Cout_sig(4),
Cout => Cout_sig(5),
Gout => Gout_sig(5)
);

CAR06:Arith_fullAdder PORT MAP(
X => out0(6),
Y => '0',

```

```

Cin => Cout_sig(5),
Cout => Cout_sig(6),
Gout => Gout_sig(6)
);

```

```

CAR07:Arith_fullAdder PORT MAP(
X => out0(7),
Y => '0',
Cin => Cout_sig(6),
Cout => Cout_sig(7),
Gout => Gout_sig(7)
);

```

```

process(Clk)
begin
  if reset = '1' then out0 <= "00000000";
  end if;
  if(falling_edge(Clk)) then
    --if sel = 'U' then out0 <= "00000000";
    if sel = '0' then out0 <= Gout_sig;
    elsif sel = '1' then out0 <= in0;
    end if;
  end if;
  end process;
end Behavioral;

```

TESTBENCH

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

-- Uncomment the following library declaration if
using
-- arithmetic functions with Signed or Unsigned
values
--USE ieee.numeric_std.ALL;

```

```

ENTITY CARTest IS
END CARTest;

```

```

ARCHITECTURE behavior OF CARTest IS

```

```

    -- Component Declaration for the Unit Under Test
    (UUT)

```

```

    COMPONENT control_access_reg
    PORT(

```

```

        in0 : IN  std_logic_vector(7 downto 0);
        sel : IN  std_logic;
            reset : in std_logic;
            Clk : in std_logic;
        out0 : inout std_logic_vector(7 downto 0)
    );
END COMPONENT;

--Inputs
    signal in0 : std_logic_vector(7 downto 0) :=
(others => '0');
    signal sel : std_logic := '0';
    signal Clk : std_logic := '0';
    signal reset : std_logic := '0';

    --Outputs
    signal out0 : std_logic_vector(7 downto 0);
    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

    constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: control_access_reg PORT MAP (
        in0 => in0,
        sel => sel,
        out0 => out0,
        reset => reset,
        Clk => Clk
    );

    --Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin

```

```

-- hold reset state for 100 ns.
wait for 100 ns;
sel <= 'U';
    reset <= '1';
    assert out0 <= "00000000";
    wait for 10ns;
    reset <= '0';

    sel <= '1';
    wait for 10ns;
    assert out0 = "00000110";

    wait for Clk_period*10;

    wait;
end process;

END;

CONTROL MEMORY

CODE
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity control_memory is
Port ( MW : out std_logic;
      MM : out std_logic;
      RW : out std_logic;
      MD : out std_logic;
      FS : out std_logic_vector(4 downto 0);
      MB : out std_logic;
      TB : out std_logic;
      TA : out std_logic;
      TD : out std_logic;
      PL : out std_logic;
      PI : out std_logic;
      IL : out std_logic;
      MC : out std_logic;
      MS : out std_logic_vector(2 downto 0);
      NA : out std_logic_vector(7 downto 0);
      IN_CAR : in std_logic_vector(7 downto 0));
end control_memory;

architecture Behavioral of control_memory is
type mem_array is array(0 to 255) of

```

```

std_logic_vector(27 downto 0);
begin
memory_m: process(IN_CAR)
variable control_mem : mem_array:=
--0
X"000001F", -- 0 - transfer 16 0's to R0, a/b data
outputs all 0's
X"000001F", -- 1
X"000001F", -- 2
X"0000000", -- 3
X"BBBBBBB", -- 4
X"0000000", -- 5
X"CCCCCCC", -- 6
X"0000000", -- 7
X"DDDDDDD", -- 8
X"0000000", -- 9
X"1111111", -- A
X"0000000", -- B
X"2222222", -- C
X"0000000", -- D
X"3333333", -- E
X"0000000", -- F

-- 1
X"0000000", -- 0
X"0000000", -- 1
X"0000000", -- 2
X"0000000", -- 3
X"0000000", -- 4
X"0000000", -- 5
X"0000000", -- 6
X"0000000", -- 7
X"0000000", -- 8
X"0000000", -- 9
X"0000000", -- A
X"0000000", -- B
X"0000000", -- C
X"0000000", -- D
X"0000000", -- E
X"0000000", -- F

-- 2
X"0000000", -- 0
X"0000000", -- 1
X"0000000", -- 2
X"0000000", -- 3
X"0000000", -- 4
X"0000000", -- 5

```



```
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 3
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 4
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 5
```

```
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 6
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 7
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
```

```
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 8
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- 9
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- A
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
```

```
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- B
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- C
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- D
```

```
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- E
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
X"00000000", -- C
X"00000000", -- D
X"00000000", -- E
X"00000000", -- F
```

```
-- F
X"00000000", -- 0
X"00000000", -- 1
X"00000000", -- 2
X"00000000", -- 3
X"00000000", -- 4
X"00000000", -- 5
X"00000000", -- 6
X"00000000", -- 7
X"00000000", -- 8
X"00000000", -- 9
X"00000000", -- A
X"00000000", -- B
```

```

X"0000000", -- C
X"0000000", -- D
X"0000000", -- E
X"0000000"  -- F
);
variable addr : integer;
variable control_out : std_logic_vector(27 downto 0);

```

```

begin
addr := conv_integer(IN_CAR);
control_out := control_mem(addr);
    MW <= control_out(0);
    MM <= control_out(1);
    RW <= control_out(2);
    MD <= control_out(3);
    FS <= control_out(8 downto 4);
    MB <= control_out(9);
    TB <= control_out(10);
    TA <= control_out(11);
    TD <= control_out(12);
    PL <= control_out(13);
    PI <= control_out(14);
    IL <= control_out(15);
    MC <= control_out(16);
    MS <= control_out(19 downto 17);
    NA <= control_out(27 downto 20);
end process;

```

```

end Behavioral;

```

```

TESTBENCH

```

```

ENTITY ControlMemoryTest IS
END ControlMemoryTest;

```

```

ARCHITECTURE behavior OF ControlMemoryTest IS

```

```

    -- Component Declaration for the Unit Under Test
    (UUT)

```

```

COMPONENT control_memory
PORT(
    MW : OUT    std_logic;
    MM : OUT    std_logic;
    RW : OUT    std_logic;
    MD : OUT    std_logic;
    FS : OUT    std_logic_vector(4 downto 0);
    MB : OUT    std_logic;

```

```

        TB : OUT    std_logic;
        TA : OUT    std_logic;
        TD : OUT    std_logic;
        PL : OUT    std_logic;
        PI : OUT    std_logic;
        IL : OUT    std_logic;
        MC : OUT    std_logic;
        MS : OUT    std_logic_vector(2 downto 0);
        NA : OUT    std_logic_vector(7 downto 0);
        IN_CAR : IN  std_logic_vector(7 downto 0)
    );
END COMPONENT;

--Inputs
signal IN_CAR : std_logic_vector(7 downto 0) :=
(others => '0');

--Outputs
signal MW : std_logic;
signal MM : std_logic;
signal RW : std_logic;
signal MD : std_logic;
signal FS : std_logic_vector(4 downto 0);
signal MB : std_logic;
signal TB : std_logic;
signal TA : std_logic;
signal TD : std_logic;
signal PL : std_logic;
signal PI : std_logic;
signal IL : std_logic;
signal MC : std_logic;
signal MS : std_logic_vector(2 downto 0);
signal NA : std_logic_vector(7 downto 0);
-- No clocks detected in port list. Replace
<clock> below with
-- appropriate port name

--constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: control_memory PORT MAP (
        MW => MW,
        MM => MM,
        RW => RW,
        MD => MD,

```

```

        FS => FS,
        MB => MB,
        TB => TB,
        TA => TA,
        TD => TD,
        PL => PL,
        PI => PI,
        IL => IL,
        MC => MC,
        MS => MS,
        NA => NA,
        IN_CAR => IN_CAR
    );

-- Clock process definitions
--<clock>_process :process
--begin
    --<clock> <= '0';
    --wait for <clock>_period/2;
    --<clock> <= '1';
    --wait for <clock>_period/2;
--end process;

-- Stimulus process
stim_proc: process
begin

    wait for 100 ns;
    --wait for <clock>_period*10;
    IN_CAR <= "00000010";
    wait for 50ns;

    wait;
end process;

END;

REGISTER FILE 9X16

CODE
entity Register_file is
    Port ( s0_Amux9to16 : in   STD_LOGIC_VECTOR(2
DOWNTO 0);
           s0_Bmux9to16 : in   STD_LOGIC_VECTOR(2
DOWNTO 0);
           s0_dec3to9  : in   STD_LOGIC_VECTOR(2 DOWNTO
0);

```



```

        TD : in STD_LOGIC;
        TA : in STD_LOGIC;
        TB : in STD_LOGIC;
        loadEnable : in STD_LOGIC;
DData      : in STD_LOGIC_VECTOR(15
DOWNTO 0);
        Clk : in STD_LOGIC;
        Adata : out STD_LOGIC_VECTOR(15 DOWNTO
0);
        Bdata : out STD_LOGIC_VECTOR(15 DOWNTO 0)
);
end Register_file;

```

**architecture** Behavioral **of** Register\_file **is**  
--components

```

    --16 bit register for register file
    component reg
Port ( load : in STD_LOGIC;
      Clk : in STD_LOGIC;
      in0 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
      out0 : out STD_LOGIC_VECTOR(15 DOWNTO 0)
);
    end component;

    --AND gate to control decoder to register load
bit
    component load_reg
Port ( in0 : in STD_LOGIC;
      in1 : in STD_LOGIC;
      out0 : out STD_LOGIC
);
    end component;

    --A Data 16 bit 9 to 1 multiplexor
    component Amux_9to16bit
Port (
        in0 : in STD_LOGIC_VECTOR(15 DOWNTO
0);
        in1 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in2 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in3 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in4 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in5 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in6 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in7 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
        in8 : in STD_LOGIC_VECTOR(15 DOWNTO
0);

```

```

        TA : in STD_LOGIC;
        s0 : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
        out0 : out STD_LOGIC_VECTOR(15 DOWNTO 0)
            );
    end component;

--B Data 16 bit 9 to 1 multiplexor
    component Bmux_9to16bit
    Port (
        in0 : in  STD_LOGIC_VECTOR(15 DOWNTO
0);
        in1 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in2 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in3 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in4 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in5 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in6 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in7 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in8 : in  STD_LOGIC_VECTOR(15 DOWNTO
0);
        TB : in STD_LOGIC;
        s0 : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
        out0 : out STD_LOGIC_VECTOR(15 DOWNTO 0)
            );
    end component;

--1 bit 3 to 9 decoder
    component Decoder_3to9
    Port (
        in0 : in  STD_LOGIC_VECTOR(2 downto
0);
        TD : in STD_LOGIC;
        out0 : out STD_LOGIC_VECTOR(8 downto 0)
            );
    end component;

-- signals. and to reg, dec to and, reg to mux
    signal load_reg0, load_reg1, load_reg2, load_reg3,
        load_reg4, load_reg5, load_reg6, load_reg7,
        load_reg8 : std_logic;
    signal selDec_reg0, selDec_reg1, selDec_reg2,
        selDec_reg3,
        selDec_reg4, selDec_reg5, selDec_reg6,
        selDec_reg7, selDec_reg8 : std_logic;
    signal reg0_sig, reg1_sig, reg2_sig, reg3_sig,
        reg4_sig,
        reg5_sig, reg6_sig, reg7_sig, reg8_sig,
        mux_2to16bit_sig,

```

```
Amux_9to16bit_sig, Bmux_9to16bit_sig :  
std_logic_vector(15 downto 0);
```

```
begin
```

```
gate00:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg0,  
    out0 => load_reg0  
);
```

```
gate01:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg1,  
    out0 => load_reg1  
);
```

```
gate02:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg2,  
    out0 => load_reg2  
);
```

```
gate03:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg3,  
    out0 => load_reg3  
);
```

```
gate04:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg4,  
    out0 => load_reg4  
);
```

```
gate05:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg5,  
    out0 => load_reg5  
);
```

```
gate06:load_reg PORT MAP(  
    in0 => loadEnable,  
    in1 => selDec_reg6,  
    out0 => load_reg6  
);
```

```
gate07:load_reg PORT MAP(  
    in0 => loadEnable,
```

```

in1 => selDec_reg7,
out0 => load_reg7
);

gate08:load_reg PORT MAP(
in0 => loadEnable,
in1 => selDec_reg8,
out0 => load_reg8
);

reg00:reg PORT MAP(
in0 => DData,
load => load_reg0,
Clk => Clk,
out0 => reg0_sig
);

reg01:reg PORT MAP(
in0 => DData,
load => load_reg1,
Clk => Clk,
out0 => reg1_sig
);

reg02:reg PORT MAP(
in0 => DData,
load => load_reg2,
Clk => Clk,
out0 => reg2_sig
);

reg03:reg PORT MAP(
in0 => DData,
load => load_reg3,
Clk => Clk,
out0 => reg3_sig
);

reg04:reg PORT MAP(
in0 => DData,
load => load_reg4,
Clk => Clk,
out0 => reg4_sig
);

reg05:reg PORT MAP(
in0 => DData,
load => load_reg5,

```

```

Clk => Clk,
out0 => reg5_sig
);

reg06:reg PORT MAP(
in0 => DData,
load => load_reg6,
Clk => Clk,
out0 => reg6_sig
);

reg07:reg PORT MAP(
in0 => DData,
load => load_reg7,
Clk => Clk,
out0 => reg7_sig
);

reg08:reg PORT MAP(
in0 => DData,
load => load_reg8,
Clk => Clk,
out0 => reg8_sig
);

--decoder port map
decoder:Decoder_3to9 PORT MAP(
    in0 => s0_dec3to9,
    out0(0) => selDec_reg0,
    out0(1) => selDec_reg1,
    out0(2) => selDec_reg2,
    out0(3) => selDec_reg3,
    out0(4) => selDec_reg4,
    out0(5) => selDec_reg5,
    out0(6) => selDec_reg6,
    out0(7) => selDec_reg7,
    out0(8) => selDec_reg8,
    TD => TD
);

--A data mux 8 to 16 bit port map
Amux9to16:Amux_9to16bit PORT MAP(
    s0 => s0_Amux9to16,
    in0 => reg0_sig,
    in1 => reg1_sig,
    in2 => reg2_sig,
    in3 => reg3_sig,
    in4 => reg4_sig,

```

```

        in5 => reg5_sig,
        in6 => reg6_sig,
        in7 => reg7_sig,
        in8 => reg7_sig,
        out0 => Amux_9to16bit_sig,
        TA => TA
    );

    --B data mux 8 to 16 bit port map
    Bmux9to16:Bmux_9to16bit PORT MAP(
        s0 => s0_Bmux9to16,
        in0 => reg0_sig,
        in1 => reg1_sig,
        in2 => reg2_sig,
        in3 => reg3_sig,
        in4 => reg4_sig,
        in5 => reg5_sig,
        in6 => reg6_sig,
        in7 => reg7_sig,
        in8 => reg8_sig,
        out0 => Bmux_9to16bit_sig,
        TB => TB
    );

    Adata <= Amux_9to16bit_sig;
    Bdata <= Bmux_9to16bit_sig;

```

**end** Behavioral;

TESTBENCH

**ENTITY** registerFileTest **IS**  
**END** registerFileTest;

**ARCHITECTURE** behavior **OF** registerFileTest **IS**

    -- Component Declaration for the Unit Under Test  
 (UUT)

```

    COMPONENT Register_file
    PORT(
        s0_Amux9to16 : IN  std_logic_vector(2 downto
0);
        s0_Bmux9to16 : IN  std_logic_vector(2 downto
0);
        s0_dec3to9   : IN  std_logic_vector(2 downto
0);
        loadEnable   : IN  std_logic;
        TD           : in STD_LOGIC;

```

```

        TA : in STD_LOGIC;
        TB : in STD_LOGIC;
        DData : IN std_logic_vector(15 downto 0);
        Clk : IN std_logic;
        Adata : OUT std_logic_vector(15 downto 0);
        Bdata : OUT std_logic_vector(15 downto 0)
    );
END COMPONENT;

--Inputs
signal s0_Amux9to16 : std_logic_vector(2 downto 0)
:= (others => '0');
signal s0_Bmux9to16 : std_logic_vector(2 downto 0)
:= (others => '0');
signal s0_dec3to9 : std_logic_vector(2 downto 0)
:= (others => '0');
signal loadEnable : std_logic := '0';
signal DData : std_logic_vector(15 downto 0) :=
(others => '0');
signal Clk : std_logic := '0';
SIGNAL TD : std_logic := '0';
SIGNAL TA : std_logic := '0';
SIGNAL TB : std_logic := '0';

--Outputs
signal Adata : std_logic_vector(15 downto 0);
signal Bdata : std_logic_vector(15 downto 0);

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Register_file PORT MAP (
        s0_Amux9to16 => s0_Amux9to16,
        s0_Bmux9to16 => s0_Bmux9to16,
        s0_dec3to9 => s0_dec3to9,
        loadEnable => loadEnable,
        DData => DData,
        TD => TD,
        TA => TA,
        TB => TB,
        Clk => Clk,
        Adata => Adata,
        Bdata => Bdata
    );

```

```

-- Clock process definitions
Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;
    DData <= "1111111111111111";
    TD <= '0';
    TA <= '0';
    TB <= '0';
    s0_dec3to9 <= "000";
    loadEnable <= '1';
    s0_Amux9to16 <= "000";
    s0_Bmux9to16 <= "000";
    wait for 20ns;

    assert AData = "1111111111111111";
    assert BData = "1111111111111111";

    wait for Clk_period*10;

    -- insert stimulus here

    wait;
end process;

END;

ZERO_FILL

CODE

entity zeroFill is
Port ( in0 : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
      out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
      );
end zeroFill;

architecture Behavioral of zeroFill is

```



```

begin
    out0(15 downto 3) <= "00000000000000";
    out0(2 downto 0) <= in0;

end Behavioral;

TESTBENCH
ENTITY zeroFillTest IS
END zeroFillTest;

ARCHITECTURE behavior OF zeroFillTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT zeroFill
    PORT(
        in0 : IN  std_logic_vector(2 downto 0);
        out0 : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal in0 : std_logic_vector(2 downto 0) :=
    (others => '0');

    --Outputs
    signal out0 : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

    --constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: zeroFill PORT MAP (
        in0 => in0,
        out0 => out0
    );

    -- Clock process definitions
    --<clock>_process :process
    --begin
        --<clock> <= '0';

```

```

        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        in0 <= "101";
        wait for 10ns;
        assert out0 <= "00000000000000101";

        --wait for <clock>_period*10;
        -- insert stimulus here

        wait;
    end process;

END;

B MUX

CODE
entity Datapath_Bmux2to1 is
    Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          in1 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          S : in  STD_LOGIC;
          out0 : out  STD_LOGIC_VECTOR(15 DOWNT0 0)
        );
end Datapath_Bmux2to1;

architecture Behavioral of Datapath_Bmux2to1 is

begin
    out0 <= in0 when S <= '0' else
        in1 when S <= '1';

end Behavioral;


```

TESTBENCH

```

ENTITY Datapath_Bmux2to1Test IS
END Datapath_Bmux2to1Test;

```

**ARCHITECTURE** behavior **OF** Datapath\_Bmux2to1Test **IS**

-- Component Declaration for the Unit Under Test  
(UUT)

**COMPONENT** Datapath\_Bmux2to1

**PORT**(

in0 : **IN** std\_logic\_vector(15 **downto** 0);

in1 : **IN** std\_logic\_vector(15 **downto** 0);

S : **IN** std\_logic;

out0 : **OUT** std\_logic\_vector(15 **downto** 0)

);

**END COMPONENT**;

--Inputs

**signal** in0 : std\_logic\_vector(15 **downto** 0) :=  
(**others** => '0');

**signal** in1 : std\_logic\_vector(15 **downto** 0) :=  
(**others** => '0');

**signal** S : std\_logic := '0';

--Outputs

**signal** out0 : std\_logic\_vector(15 **downto** 0);

-- No clocks detected in port list. Replace  
<clock> below with

-- appropriate port name

--constant <clock>\_period : time := 10 ns;

**BEGIN**

-- Instantiate the Unit Under Test (UUT)

uut: Datapath\_Bmux2to1 **PORT MAP** (

in0 => in0,

in1 => in1,

S => S,

out0 => out0

);

-- Clock process definitions

--<clock>\_process :process

--begin

--<clock> <= '0';

--wait for <clock>\_period/2;

--<clock> <= '1';

--wait for <clock>\_period/2;

--end process;

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    in0 <= "0000000000000000";
    in1 <= "1111111111111111";

    S <= '0';
    wait for 10ns;
    assert out0 <= "0000000000000000";

    S <= '1';
    wait for 10ns;
    assert out0 <= "1111111111111111";

    --wait for <clock>_period*10;
    -- insert stimulus here
    wait;
end process;

END;

MUX M

CODE
entity MUX_M is
    Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          in1 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          sel : in  STD_LOGIC;
          out0 : out STD_LOGIC_VECTOR(15 DOWNT0 0)
        );
    end MUX_M;

architecture Behavioral of MUX_M is

begin
    out0 <= in0 when sel = '0' else
            in1 when sel = '1';

end Behavioral;

TESTBENCH

```

```

ENTITY MUX_MTest IS
END MUX_MTest;

ARCHITECTURE behavior OF MUX_MTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT MUX_M
    PORT(
        in0 : IN    std_logic_VECTOR(15 DOWNTO 0);
        in1 : IN    std_logic_VECTOR(15 DOWNTO 0);
        sel : IN    std_logic;
        out0 : OUT  std_logic_VECTOR(15 DOWNTO 0)
    );
    END COMPONENT;

    --Inputs
        signal in0 : std_logic_vector(15 downto 0) :=
(others => '0');
        signal in1 : std_logic_vector(15 downto 0) :=
(others => '0');
        signal sel : std_logic := '0';

    --Outputs
        signal out0 : std_logic_vector(15 downto 0) :=
(others => '0');

    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

    --constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: MUX_M PORT MAP (
        in0 => in0,
        in1 => in1,
        sel => sel,
        out0 => out0
    );

    -- Clock process definitions
    --<clock>_process :process
    --begin

```

```

        --<clock> <= '0';
        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

    -- Stimulus process
    stim_proc: process
    begin
        wait for 100 ns;
        in0 <= "0000000000000000";
        in1 <= "1111111111111111";

        sel <= '0';
        wait for 10ns;
        assert out0 = "0000000000000000";

        sel <= '1';
        wait for 10ns;
        assert out0 = "1111111111111111";

        wait;
    end process;

END;

FUNCTION UNIT

CODE
entity FunctionUnit_16bit is
    Port ( A : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
          B : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
          FSselect : in  STD_LOGIC_VECTOR(4 DOWNTO
0);

          C : out STD_LOGIC;
          V : out STD_LOGIC;
          N : out STD_LOGIC;
          Z : out STD_LOGIC;
          F : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
          );
end FunctionUnit_16bit;

architecture Behavioral of FunctionUnit_16bit is

    component ALU_16bit

```

```

Port ( A : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
      B : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
      Cin : in  STD_LOGIC;
      S : in  STD_LOGIC_VECTOR(2 DOWNT0 0);
      C : out  STD_LOGIC;
      V : out  STD_LOGIC;
      N : out  STD_LOGIC;
      Z : out  STD_LOGIC;
      G : out  STD_LOGIC_VECTOR(15 downto 0)
    );
end component;

component Shifter_16bit
Port ( B : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
      S : in  STD_LOGIC_VECTOR(1 DOWNT0 0);
      H : out  STD_LOGIC_VECTOR(15 DOWNT0 0)
    );
end component;

component FU_mux2to1
Port ( in0  : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
      in1  : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
      S    : in  STD_LOGIC;
      out0 : out  STD_LOGIC_VECTOR(15 DOWNT0 0)
    );
end component;

--signals
SIGNAL Gout_sig, Hout_sig, Fout_sig:
STD_LOGIC_VECTOR(15 DOWNT0 0);
SIGNAL Cout_sig, Vout_sig, Nout_sig, Zout_sig:
STD_LOGIC;

begin

    ALU:ALU_16bit PORT MAP(
    A => A,
    B => B,
    S(2) => FSselect(1),
    S(1) => FSselect(2),
    S(0) => FSselect(3),
    Cin => FSselect(4),
    C => Cout_sig,
    V => Vout_sig,
    N => Nout_sig,
    Z => Zout_sig,
    G => Gout_sig
    );

```

```

Shifter:Shifter_16bit PORT MAP(
B => B,
S(0) => FSselect(1),
S(1) => FSselect(2),
H => Hout_sig
);

Mux:FU_mux2to1 PORT MAP(
in0 => Gout_sig,
in1 => Hout_sig,
S => FSselect(0),
out0 => Fout_sig
);

C <= Cout_sig;
V <= Vout_sig;
N <= Nout_sig;
Z <= Zout_sig;
F <= Fout_sig;

end Behavioral;

TESTBENCH

ENTITY FunctionUnit_16bitTest IS
END FunctionUnit_16bitTest;

ARCHITECTURE behavior OF FunctionUnit_16bitTest IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT FunctionUnit_16bit
    PORT(
        A : IN    std_logic_vector(15 downto 0);
        B : IN    std_logic_vector(15 downto 0);
        FSselect : IN    std_logic_vector(4 downto 0);
        C : OUT   std_logic;
        V : OUT   std_logic;
        N : OUT   std_logic;
        Z : OUT   std_logic;
        F : OUT   std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs

```



```

    signal A : std_logic_vector(15 downto 0) :=
(others => '0');
    signal B : std_logic_vector(15 downto 0) :=
(others => '0');
    signal FSselect : std_logic_vector(4 downto 0) :=
(others => '0');

```

```

    --Outputs
    signal C : std_logic;
    signal V : std_logic;
    signal N : std_logic;
    signal Z : std_logic;
    signal F : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

```

```

    --constant <clock>_period : time := 10 ns;

```

**BEGIN**

```

    -- Instantiate the Unit Under Test (UUT)
    uut: FunctionUnit_16bit PORT MAP (
        A => A,
        B => B,
        FSselect => FSselect,
        C => C,
        V => V,
        N => N,
        Z => Z,
        F => F
    );

```

```

    -- Clock process definitions
    --<clock>_process :process
    --begin
        --<clock> <= '0';
        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

```

```

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;

```

```

A <= "0000000000000000";
B <= "1000000000000001";

--THE FS SELECTS ARE INPUTTED BACKWARDS.
--EG. 00101 IS SUBTRACT, BUT VECTOR INPUT
WILL BE "10100".
--COULD CHANGE, BUT EASIER IN THE LONG RUN.
--AS OF 2/4/2014 6:32PM ALL OF THIS SHIT
WORKS.

```

```

A <= "1000000000000001";
--INCREMENT A
FSselect <= "10000";
wait for 10ns;
assert F = "1000000000000010";
assert Z = '0';
assert V = '0';
assert N = '1';
assert C = '0';

--ADD A + B (00010)
FSselect <= "01000";
wait for 10ns;
assert F = "0000000000000010";
assert Z = '0';
assert V = '1';
assert N = '0';
assert C = '1';

--A + B + 1
FSselect <= "00011";
wait for 10ns;
assert F = "0000000000000100";

-- A + not B
B <= "1111111111111110";
FSselect <= "00100";
wait for 10ns;
assert F = "0000000000000010";

-- A - B
A <= "0000000000000010";
B <= "0000000000000001";
FSselect <= "00101";
wait for 10ns;
assert F = "0000000000000001";

```

```

-- A - 1
FSselect <= "00110";
wait for 10ns;
assert F = "0000000000000001";

-- TRANSFER A
FSselect <= "00111";
wait for 10ns;
assert F = "0000000000000010";

-- AND
FSselect <= "01000";
wait for 10ns;
assert F = "0000000000000000";

--OR
A <= "0000000000000100";
FSselect <= "01010";
wait for 10ns;
assert F = "0000000000000101";

--XOR
A <= "0000000000001000";
FSselect <= "01100";
wait for 10ns;
assert F = "0000000000001001";

--NOT A
FSselect <= "01110";
wait for 10ns;
assert F = "111111111110111";

B <= "0000000000001111";

--B TRANSFER
FSselect <= "10000";

wait for 10ns;
assert F = "0000000000001111";

--SHIFT B RIGHT
FSselect <= "10100";
wait for 10ns;
assert F = "000000000000111";

--SHIFT B LEFT
FSselect <= "11000";

```

```

        wait for 10ns;
        assert F = "0000000000011110";

        --wait for <clock>_period*10;

        -- insert stimulus here

        wait;
    end process;

END;

D MUX

CODE

entity Datapath_Dmux2to1 is
    Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          in1 : in  STD_LOGIC_VECTOR(15 DOWNT0 0);
          S  : in  STD_LOGIC;
          out0 : out STD_LOGIC_VECTOR(15 DOWNT0 0)
        );
end Datapath_Dmux2to1;

architecture Behavioral of Datapath_Dmux2to1 is

begin
    out0 <= in0 when S <= '0' else
           in1 when S <= '1';

end Behavioral;

TESTBENCH
ENTITY Datapath_Dmux2to1Test IS
END Datapath_Dmux2to1Test;

ARCHITECTURE behavior OF Datapath_Dmux2to1Test IS

    -- Component Declaration for the Unit Under Test
    (UUT)

    COMPONENT Datapath_Dmux2to1
    PORT(
        in0 : IN  std_logic_vector(15 downto 0);
        in1 : IN  std_logic_vector(15 downto 0);
        S   : IN  std_logic;
        out0 : OUT std_logic_vector(15 downto 0)
    )

```

```

    );
    END COMPONENT;

--Inputs
    signal in0 : std_logic_vector(15 downto 0) :=
(others => '0');
    signal in1 : std_logic_vector(15 downto 0) :=
(others => '0');
    signal S : std_logic := '0';

--Outputs
    signal out0 : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace
    <clock> below with
    -- appropriate port name

    --constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Datapath_Dmux2to1 PORT MAP (
        in0 => in0,
        in1 => in1,
        S => S,
        out0 => out0
    );

    -- Clock process definitions
    --<clock>_process :process
    --begin
        --<clock> <= '0';
        --wait for <clock>_period/2;
        --<clock> <= '1';
        --wait for <clock>_period/2;
    --end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        in0 <= "0000000000000000";
        in1 <= "1111111111111111";

        S <= '0';

```

```

        wait for 10ns;
        assert out0 <= "0000000000000000";

        S <= '1';
        wait for 10ns;
        assert out0 <= "1111111111111111";

        --wait for <clock>_period*10;
        -- insert stimulus here

        wait;
    end process;

END;

PROCESSER

CODE

entity Processor is
    Port ( reset : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Datapath_out: out STD_LOGIC_VECTOR(15
DOWNTO 0));
          PCouttest: out STD_LOGIC_VECTOR(15
DOWNTO 0);
          CARouttest : out STD_LOGIC_VECTOR(7
DOWNTO 0);
          TBouttest : out STD_LOGIC_VECTOR(15
downto 0)

          );
end Processor;

architecture Behavioral of Processor is

component Program_counter
Port ( in0 : in STD_LOGIC_VECTOR(15 DOWNTO 0);
      reset : IN std_logic;
      PI : in STD_LOGIC;
      PL : in STD_LOGIC;
      Clk : in STD_LOGIC;
      out0 : inout STD_LOGIC_VECTOR(15 DOWNTO 0)
      );

```

```

end component;

component extend
Port ( in0 : in  STD_LOGIC_VECTOR(5 DOWNTO 0);
      out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
      );
end component;

component NOT_cond
Port ( in0 : in  STD_LOGIC;
      in1 : in  STD_LOGIC;
      out0 : out  STD_LOGIC;
      out1 : out  STD_LOGIC);
end component;

component MUX_S
Port ( in0 : in  STD_LOGIC;
      in1 : in  STD_LOGIC;
      in2 : in  STD_LOGIC;
      in3 : in  STD_LOGIC;
      in4 : in  STD_LOGIC;
      in5 : in  STD_LOGIC;
      in6 : in  STD_LOGIC;
      in7 : in  STD_LOGIC;
      sel : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
      out0 : out  STD_LOGIC
      );
end component;

component instruction_reg
Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      sel : in  STD_LOGIC;
      opcode : out  STD_LOGIC_VECTOR(6 DOWNTO 0);
      DR : out  STD_LOGIC_VECTOR(2 DOWNTO 0);
      SA : out  STD_LOGIC_VECTOR(2 DOWNTO 0);
      Clk : in  STD_LOGIC;
      SB : out  STD_LOGIC_VECTOR(2 DOWNTO 0)
      );
end component;

component MUX_C
Port ( in0 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
      in1 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
      sel : in  STD_LOGIC;
      out0 : out  STD_LOGIC_VECTOR(7 DOWNTO 0)
      );
end component;

```

```

component control_access_reg
Port (      in0 : in  STD_LOGIC_VECTOR(7 DOWNTO 0);
          Clk  : in  STD_LOGIC;
          reset : in  STD_LOGIC;
          out0  : inout STD_LOGIC_VECTOR(7
DOWNTO 0);
          sel   : in  STD_LOGIC
        );
end component;

component control_memory
Port ( MW : out std_logic;
        MM : out std_logic;
        RW : out std_logic;
        MD : out std_logic;
        FS : out std_logic_vector(4 downto 0);
        MB : out std_logic;
        TB : out std_logic;
        TA : out std_logic;
        TD : out std_logic;
        PL : out std_logic;
        PI : out std_logic;
        IL : out std_logic;
        MC : out std_logic;
        MS : out std_logic_vector(2 downto 0);
        NA : out std_logic_vector(7 downto 0);
        IN_CAR : in std_logic_vector(7 downto 0)
        );
end component;

component zeroFill
  Port ( in0 : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
        out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
        );
end component;

component MUX_M
Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        in1 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
        sel : in  STD_LOGIC;
        out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
        );
end component;

component Memory
Port (
  address : in unsigned(15 downto 0);
  write_data : in std_logic_vector(15 downto 0);

```



```

    MW: in std_logic;
    read_data : out std_logic_vector(15 downto 0));
end component;

component register_file
Port ( s0_Amux9to16 : in  STD_LOGIC_VECTOR(2 DOWNTO
0);
      s0_Bmux9to16 : in  STD_LOGIC_VECTOR(2
DOWNTO 0);
      s0_dec3to9 : in  STD_LOGIC_VECTOR(2 DOWNTO 0);
      TD : in STD_LOGIC;
      TA : in STD_LOGIC;
      TB : in STD_LOGIC;
      loadEnable : in  STD_LOGIC;
      DData      : in  STD_LOGIC_VECTOR(15 DOWNTO
0);
      Clk : in  STD_LOGIC;
      Adata : out  STD_LOGIC_VECTOR(15 DOWNTO 0);
      Bdata : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
      );
end component;

component FunctionUnit_16bit
Port ( A : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      B : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      FSselect : in  STD_LOGIC_VECTOR(4 DOWNTO
0);
      C : out STD_LOGIC;
      N : out STD_LOGIC;
      V : out STD_LOGIC;
      Z : out STD_LOGIC;
      F : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
      );
end component;

component Datapath_Bmux2to1
Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      in1 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      S : in  STD_LOGIC;
      out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)
      );
end component;

component Datapath_Dmux2to1
Port ( in0 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      in1 : in  STD_LOGIC_VECTOR(15 DOWNTO 0);
      S : in  STD_LOGIC;
      out0 : out  STD_LOGIC_VECTOR(15 DOWNTO 0)

```

```

    );
end component;

--signals
signal MUXS_sig, not_c_sig, not_z_sig, Cout_sig,
        Nout_sig, Vout_sig, Zout_sig : STD_LOGIC;

signal DR_sig, SA_sig, SB_sig : STD_LOGIC_VECTOR(2
DOWNTO 0);

signal opcode_sig : STD_LOGIC_VECTOR(6 DOWNTO 0);

signal MUXC_sig, CAR_sig : STD_LOGIC_VECTOR(7 DOWNTO
0);

signal PCout_sig, MemMout_sig, extend_sig,
        zeroFill_sig, BusA_sig, BusB_sig,
        muxB_sig, muxM_sig, FU_sig,
        BusD_sig: STD_LOGIC_VECTOR(15 DOWNTO 0);

signal CM_sig : STD_LOGIC_VECTOR(27 DOWNTO 0);

begin
--port maps

    -- PROGRAM COUNTER
    PC:program_counter PORT MAP(
    in0 => extend_sig,
    reset => reset,
    PI => CM_sig(14),
    PL => CM_sig(13),
    Clk => Clk,
    out0 => PCout_sig
    );

    --EXTEND
    PCExtend:extend PORT MAP(
    in0(5 downto 3) => DR_sig,
    in0(2 downto 0) => SB_sig,
    out0 => extend_sig
    );

    --INVERTER
    inverter:NOT_cond PORT MAP(
    in0 => Cout_sig,
    in1 => Zout_sig,
    out0 => not_c_sig,
    out1 => not_z_sig

```

```

);

--MUX S
MUXS:MUX_S PORT MAP(
in0 => '0',
in1 => '1',
in2 => Cout_sig,
in3 => Vout_sig,
in4 => Zout_sig,
in5 => Nout_sig,
in6 => not_c_sig,
in7 => not_z_sig,
sel(0) => CM_sig(17),
sel(1) => CM_sig(18),
sel(2) => CM_sig(19),
out0 => MUXS_sig
);

--INSTRUCTION REGISTER
IR:instruction_reg PORT MAP(
in0 => MemMout_sig,
sel => CM_sig(15),
opcode => opcode_sig,
DR => DR_sig,
SA => SA_sig,
SB => SB_sig,
Clk => Clk
);

--MUX C
MUXC:MUX_C PORT MAP(
in0(0) => CM_sig(20),
in0(1) => CM_sig(21),
in0(2) => CM_sig(22),
in0(3) => CM_sig(23),
in0(4) => CM_sig(24),
in0(5) => CM_sig(25),
in0(6) => CM_sig(26),
in0(7) => CM_sig(27),
in1(6 downto 0) => opcode_sig,
in1(7) => '0',
sel => CM_sig(16),
out0 => MUXC_sig
);

--CONTROL ACCESS REGISTER
CAR:control_access_reg PORT MAP(
in0 => MUXC_sig,

```

```

        Clk => Clk,
        reset => reset,
        sel => MUXS_sig,
        out0 => CAR_sig
    );

--CONTROL MEMORY
CM:control_memory PORT MAP(
    MW => CM_sig(0),
    MM => CM_sig(1),
    RW => CM_sig(2),
    MD => CM_sig(3),
    FS(0) => CM_sig(4),
    FS(1) => CM_sig(5),
    FS(2) => CM_sig(6),
    FS(3) => CM_sig(7),
    FS(4) => CM_sig(8),
    MB => CM_sig(9),
    TB => CM_sig(10),
    TA => CM_sig(11),
    TD => CM_sig(12),
    PL => CM_sig(13),
    PI => CM_sig(14),
    IL => CM_sig(15),
    MC => CM_sig(16),
    MS(0) => CM_sig(17),
    MS(1) => CM_sig(18),
    MS(2) => CM_sig(19),
    NA(0) => CM_sig(20),
    NA(1) => CM_sig(21),
    NA(2) => CM_sig(22),
    NA(3) => CM_sig(23),
    NA(4) => CM_sig(24),
    NA(5) => CM_sig(25),
    NA(6) => CM_sig(26),
    NA(7) => CM_sig(27),
    IN_CAR => CAR_sig
);

--REGISTER FILE
registerfile:register_file PORT MAP(
    s0_dec3to9 => DR_sig,
    S0_Amux9to16 => SA_sig,
    S0_Bmux9to16 => SB_sig,
    TD => CM_sig(12),
    TA => CM_sig(11),
    TB => CM_sig(10),
    loadEnable => CM_sig(2),

```

```

    Clk => Clk,
    DData => BusD_sig,
    AData => BusA_sig,
    BData => BusB_sig
  );

  --ZERO FILL
  fillWithZero:zeroFill PORT MAP(
    in0 => SB_sig,
    out0 => zeroFill_sig
  );

  --B MUX
  MUXB:Datapath_Bmux2to1 PORT MAP(
    in0 => BusB_sig,
    in1 => zeroFill_sig,
    S => CM_sig(9),
    out0 => muxB_sig
  );

  --M MUX
  MUXM:MUX_M PORT MAP(
    in0 => busA_sig,
    in1 => PCout_sig,
    sel => CM_sig(1),
    out0 => muxM_sig
  );

  --FUNCTIONAL UNIT
  FunctionUnit:FunctionUnit_16bit PORT MAP(
    A => BusA_sig,
    B => muxB_sig,
    FSselect(4) => CM_sig(8),
    FSselect(3) => CM_sig(7),
    FSselect(2) => CM_sig(6),
    FSselect(1) => CM_sig(5),
    FSselect(0) => CM_sig(4),
    C => Cout_sig,
    N => Nout_sig,
    V => Vout_sig,
    Z => Zout_sig,
    F => FU_sig
  );

  --MEMORY M
  MemoryM:Memory PORT MAP (
    address => unsigned(muxM_sig),
    write_data => muxB_sig,

```

```

MW => CM_sig(0),
  read_data => MemMout_sig
);

--MUX D
MUXD:Datapath_Dmux2to1 PORT MAP(
  in0 => FU_sig,
  in1 => MemMout_sig,
  S => CM_sig(3),
  out0 => BusD_sig
);

CARouttest <= CAR_sig;
Datapath_out <= BusD_sig;
PCOuttest <= PCout_sig;
TBouttest <= memMout_sig;
end Behavioral;

TESTBENCH
ENTITY ProcesserTest IS
END ProcesserTest;

ARCHITECTURE behavior OF ProcesserTest IS

  -- Component Declaration for the Unit Under Test
  (UUT)

  COMPONENT Processer
  PORT(
    reset : IN std_logic;
    Clk : IN std_logic;
    Datapath_out : OUT std_logic_vector(15
downto 0);
    PCouttest : out std_logic_vector(15
downto 0);
    CARouttest : out std_logic_vector(7
downto 0);
    TBouttest : out STD_LOGIC_VECTOR(15
downto 0)
  );
  END COMPONENT;

  --Inputs
  signal reset : std_logic := '0';
  signal Clk : std_logic := '0';

```

```

--Outputs
signal TBouttest : STD_LOGIC_VECTOR(15 downto
0);
signal Datapath_out : std_logic_vector(15 downto
0);
signal PCouttest : std_logic_vector(15 downto
0);
signal CARouttest : std_logic_vector(7 downto 0);

-- Clock period definitions
constant Clk_period : time := 10 ns;

```

**BEGIN**

```

-- Instantiate the Unit Under Test (UUT)
uut: Processor PORT MAP (
    reset => reset,
    Clk => Clk,
    Datapath_out => Datapath_out,
    PCouttest => PCouttest,
    CARouttest => CARouttest,
    TBouttest => TBouttest

);

```

```

-- Clock process definitions
Clk_process :process
begin
    Clk <= '0';
    wait for Clk_period/2;
    Clk <= '1';
    wait for Clk_period/2;
end process;

```

```

-- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
    wait for 100 ns;

    reset <= '1';
    wait for 10ns;
    reset <= '0';


    -- insert stimulus here

    wait;


```

**end process;**

**END;**

 


## D MUX 2 TO 1 WAVEFORM

 


## CAR WAVEFORM




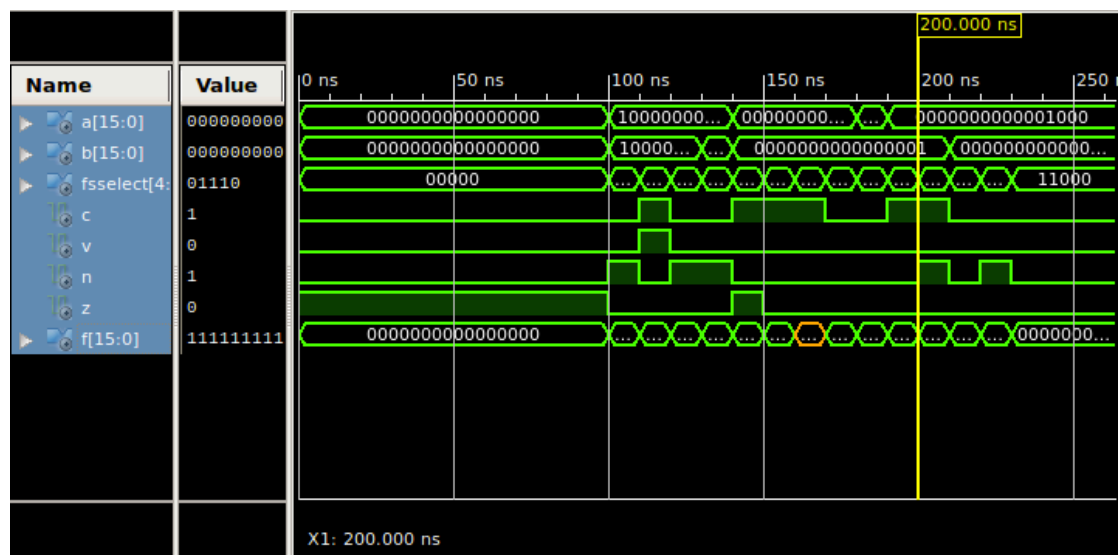


## FUNCTIONAL UNIT WAVEFORM

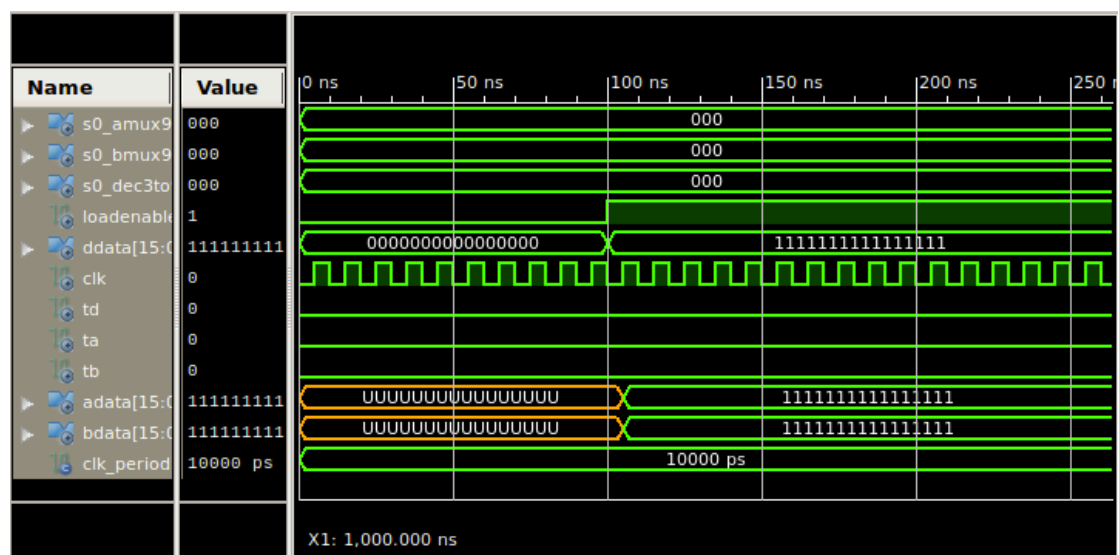


## REGISTER FILE WAVEFORM

 


ZERO FILL WAVEFORM

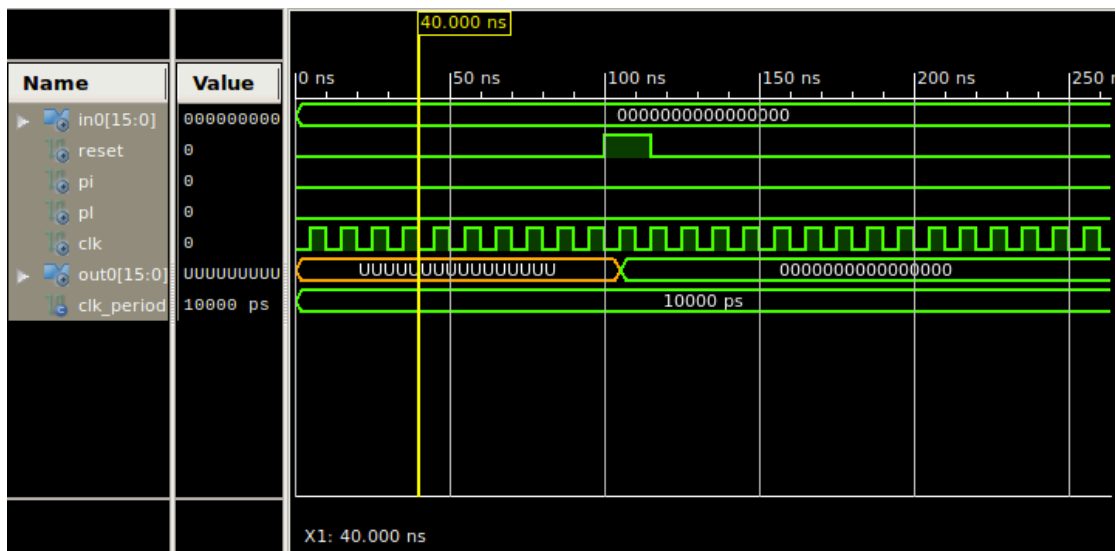


PROGRAM COUNTER WAVEFORM

 


### INVERTER WAVEFORM

 


### EXTEND WAVEFORM

 


MEMORY WAVEFORM

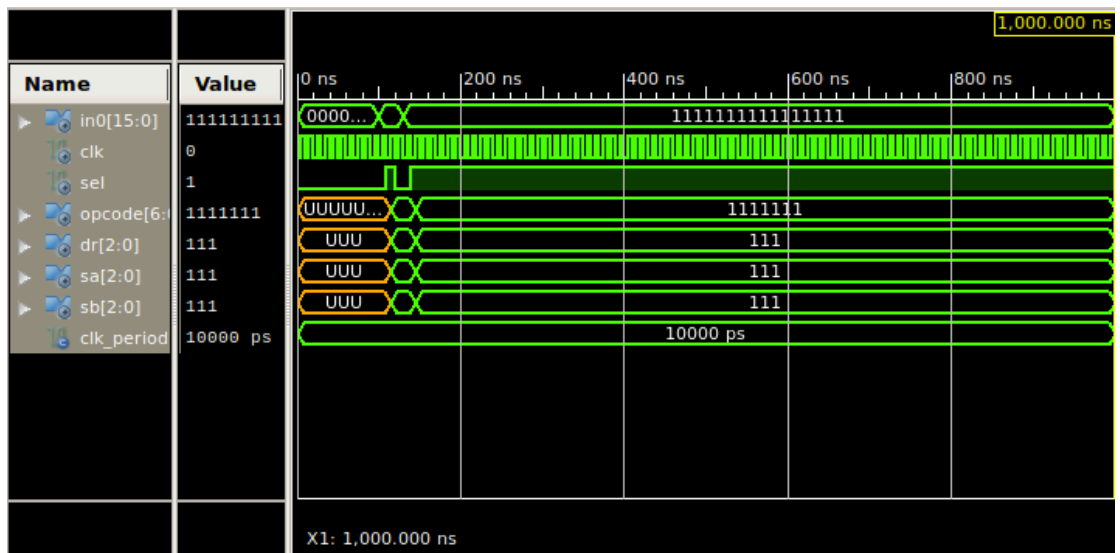

INSTRUCTION REGISTER WAVEFORM

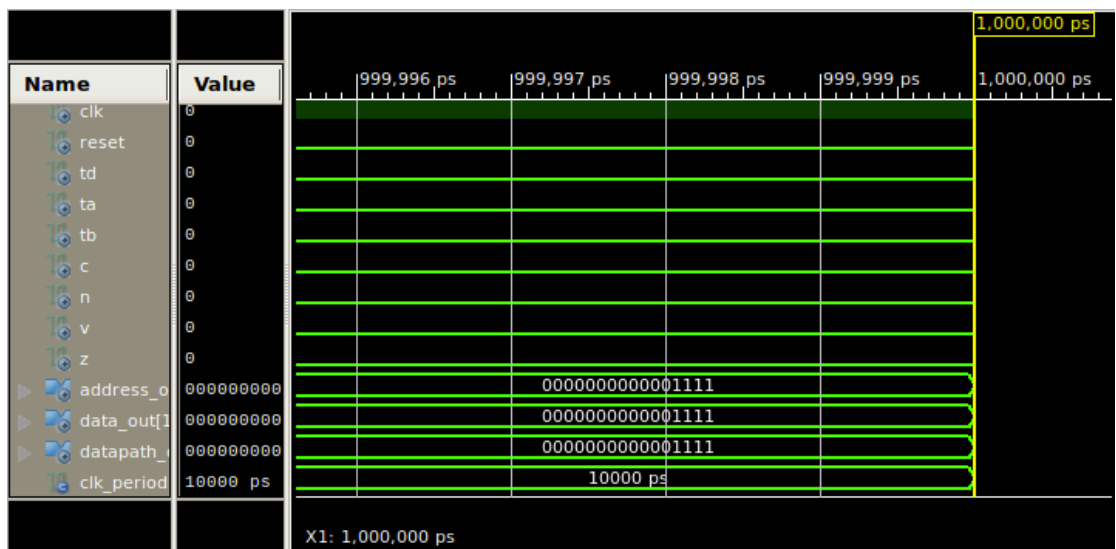

DATAPATH WAVEFORM

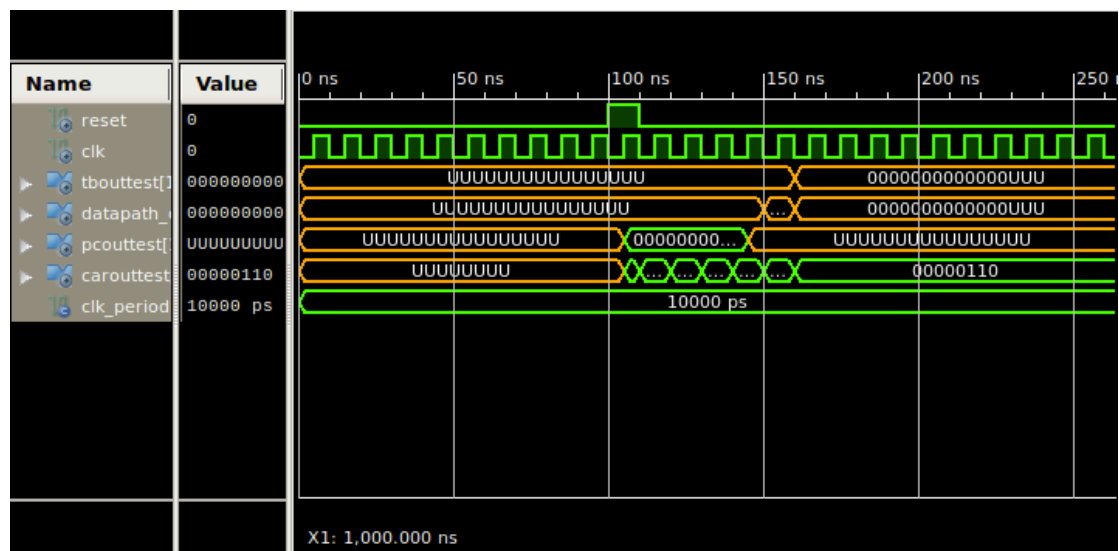

PROCESSOR WAVEFORM